



UNIVERSITY OF TEHRAN
Electrical and Computer Engineering Department
Digital Logic Design, ECE 367, Spring 1400
Computer Assignment 3
RT Level Components, Iterative Logic, Synthesis - Week 12

Name:

Date:

Username:

The problem for this assignment is a circuit that calculates the number of 1's on its data inputs. The circuit that is to be designed has 127 inputs, and it is built of cascadable modules in a regular structure.

1. Show the design of a full-adder using basic gate structures. Using the delay values from transistors of Computer Assignment 1, estimate the worst-case gate delays of your full-adder structure. Write a parameterized full-adder and use the delay values in this SystemVerilog description. Simulate this structure and verify your worst-case delay values.
2. Based on delay values of the full-adder of Part 1, write a parametrized n-bit adder that uses n to adjust the size and delay value of the adder. The adder module uses **#parameter(...)** construct in its header part. For the delay values assume the adder is realized as a Ripple-carry adder. You can use an **assign** statement for this description. No need to do a structural description based on the full-adder.
3. Test the adder of Part 2 for n value of 4 using a SystemVerilog testbench. Use constructs such as **repeat** and **\$random()** for test data generation.
4. Using SystemVerilog **generate** statement wire n-bit adders (where n is 1 to 6) in a tree structure to build a 127-bit one's counter.
5. Test your design of Part 4 for functionality and timing using a SystemVerilog testbench. Among other tests, in the testbench generate a 127 bit Marching-1 data generator for providing data to your counter.
6. Using SystemVerilog **always** and procedural **for** statements write a synthesizable description of the One's Counter of Part 4. Annotate this description with delays obtained from the SystemVerilog of Part 4. Run simulations and compare results.
7. Using YoSys synthesize the circuit of Part 4 and that of Part 6 and compare the results.